

قسم هندسة تقنيات الحاسوب
التاريخ : 2024 / 4 / 21
وقت الامتحان : 90 دقيقة

الامتحان المشترك 2024/2023
Subject: الكترونك

وزارة التعليم العالي والبحث العلمي
الجامعة التقنية الوسطى
الكلية التقنية الهندسية الكهربائية

Answer All Questions, the Questions are in TWO Pages

1) For the circuit shown in Fig (1):

R_{th} (in Fig 1) =

- (A) 5.324 K Ω (B) 6 K Ω (C) 3.54 K Ω (D) 3.45 K Ω

2) E_{th} (in Fig 1) =

- (A) 2v (B) 3v (C) 1v (D) 4v

3) The condition for using the approximate technique in voltage divider bias is

- (A) $\beta R_C \geq R_E$ (B) $\beta R_E \leq R_B$

- (C) $\beta R_E \geq 10R_2$ (D) $\beta R_B \geq 10R_2$

4) I_B (in Fig 1) =

- (A) 5.38 μA (B) 1.83 μA (C) 8.38 μA (D) 4.29 μA

5. The phase difference between the output and input voltages of a CE amplifier is

- (A) 180° (B) 0° (C) 90° (D) 270°

6. For the fixed bias BJT configuration If $V_{CC}=12$ v, $I_C=2.35$ mA and $R_C=2.2$ K Ω , $V_{CE}=$

- (A) 17.17 v (B) 4.2 v (C) -5.3 v (D) 6.83 v

7) For the network of Fig(2) below, if $I_E=1.3$ mA, $r_e =$:

- (A) 2 Ω (B) 8 Ω (C) 15 Ω (D) 20 Ω

8) The input impedance Z_i (in Fig 2) =

- (A) 20 Ω (B) 19.61 Ω (C) 1.8 Ω (D) 40.2 Ω

9) The voltage gain A_v (in Fig2) =

- (A) 150 (B) 100 (C) 250 (D) 80

10) The current gain A_i (in Fig2) =

- (A) -0.98 (B) -0.99 (C) -1 (D) -100

11) Which resistor in a voltage divider configuration with a BJT transistor determines the output voltage?

- (A) Base resistor (B) Collector resistor (C) Emitter resistor (D) Load resistor



12) For the fixed-bias JFET if $I_D=10$ mA, $V_{DD}=20$ v $R_D=1.5$ K Ω what is the value of the V_{DS} ?

- (A) 7.5 V (B) 4 V (C) 5.75 V (D) 5 V

13) The Shockley equation is

(A) $I_D = I_{DSS} [1 - \frac{V_{GS}}{V_p}]^2$ (B) $I_D = I_{DSS} [1 - \frac{V_{GS}}{V_p}]^3$

  (C) $I_D = I_{DSS} [2 - \frac{V_{GS}}{V_p}]^2$ (D) $I_D = I_{DSS} [1 - \frac{V_{GS}}{V_p}]^3$



قسم هندسة تقنيات الحاسوب
التاريخ: 2024 / 4 / 21
وقت الامتحان: 90 دقيقة

الامتحان المشترك 2024/2023
Subject: الكرونوك

وزارة التعليم العالي والبحث العلمي
الجامعة التقنية الوسطى
الكلية التقنية الهندسية الكهربائية

14) For a voltage divider bias $A_{v\text{mid}}$

- (A) $\frac{R_c}{r_e}$ (B) $\frac{R_c}{r_e + R_E}$ (C) $\frac{R_B}{R_B + Z_b}$ (D) $\frac{\beta R_B}{R_B + Z_b}$

15) The Field Effect Transistor is called in this name because:

- (A) Drain Current is controlled due to electric field V_{gs} (C) It is a unipolar device
(B) FET is smaller in size than BJT (D) FET has very high input impedance

16) The ac equivalent of a transistor network is obtained by Replacing all capacitors by-----

- (A) Open circuit (B) short-circuit (C) Bypass capacitor (D) none of the above

17) Which of BJT transistor currents is the largest?

- (A) I_C (B) I_E (C) I_B (D) I_D

18) Which of FET transistor currents should always be = 0?

- (A) I_D (B) I_S (C) I_G (D) I_B

19) A JFET data sheet specifies $V_P = -10\text{ V}$ and $I_{DSS} = 8\text{ mA}$. Find the value of I_D when $V_{GS} = -3\text{ V}$.

- (A) 2 mA (B) 1.4 mA (C) 4.8 mA (D) 3.92 mA

20) For all FETs

- (A) $I_D = I_S$ (B) $I_D = 0\text{ mA}$ (C) $I_D = I_G$ (D) $I_S = I_G$

21) In re model of C.B. configuration $Z_o =$

- (A) ∞ (B) β (C) 0 (D) None of above

22) Given $\beta = 120$ and $I_E = 3.2\text{ mA}$ for a common-emitter configuration with $r_o = \infty\ \Omega$. Determine Z_i .

- (A) 975k Ω (B) 0k Ω (C) 5k Ω (D) 1.2 k Ω

23) For an n-channel FET, What is the direction of current flow

- (A) Source to drain (B) Drain to source
(C) Gate to source (D) Gate to drain

24) For the fixed-bias JFET with $I_{DSS} = 10\text{ mA}$, $V_P = -8\text{ v}$ and $V_{GG} = 2\text{ v}$, what is the value of the drain current I_D ?

- (A) 6.250 mA (B) 2.650 mA (C) 5.625 mA (D) 100

25) For the FET transfer characteristics when $I_D = I_{DSS}$, then V_{GS} is

- (A) -1.8 V (B) -3V (C) 0 V (D) -6V