



Experiment Two Diode Applications



Part One: Half-wave Rectifier

AIM: To study the input signal in the diode and the output signal from it, then calculate the output d.c voltage.

Apparatus: Virtual diode, A.C power source = (14.14 rms and 50 Hz), Resistance = 1 kΩ, Ground, Oscilloscope and Multimeter.

Circuit diagram:

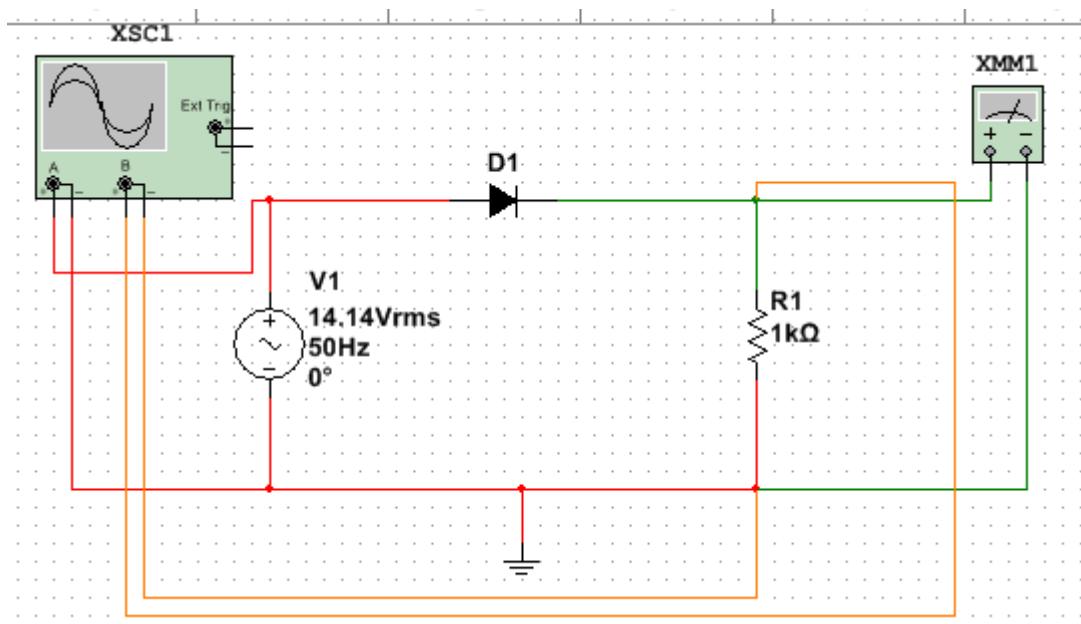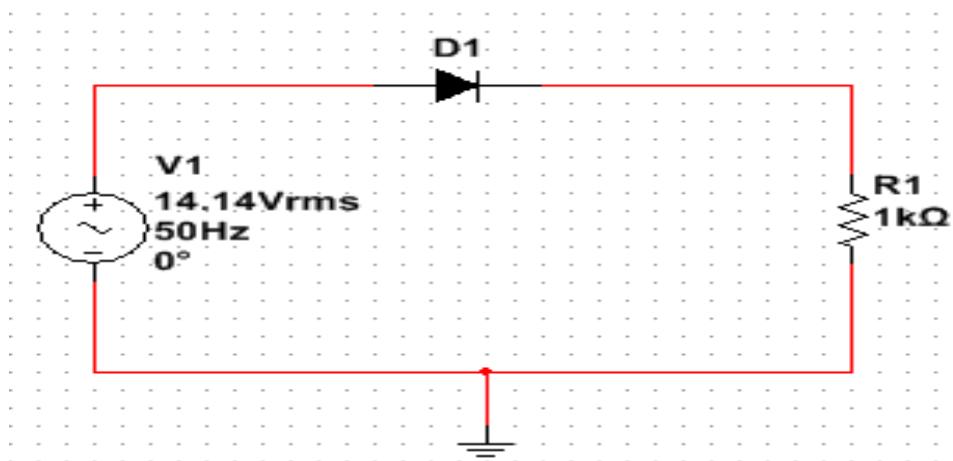

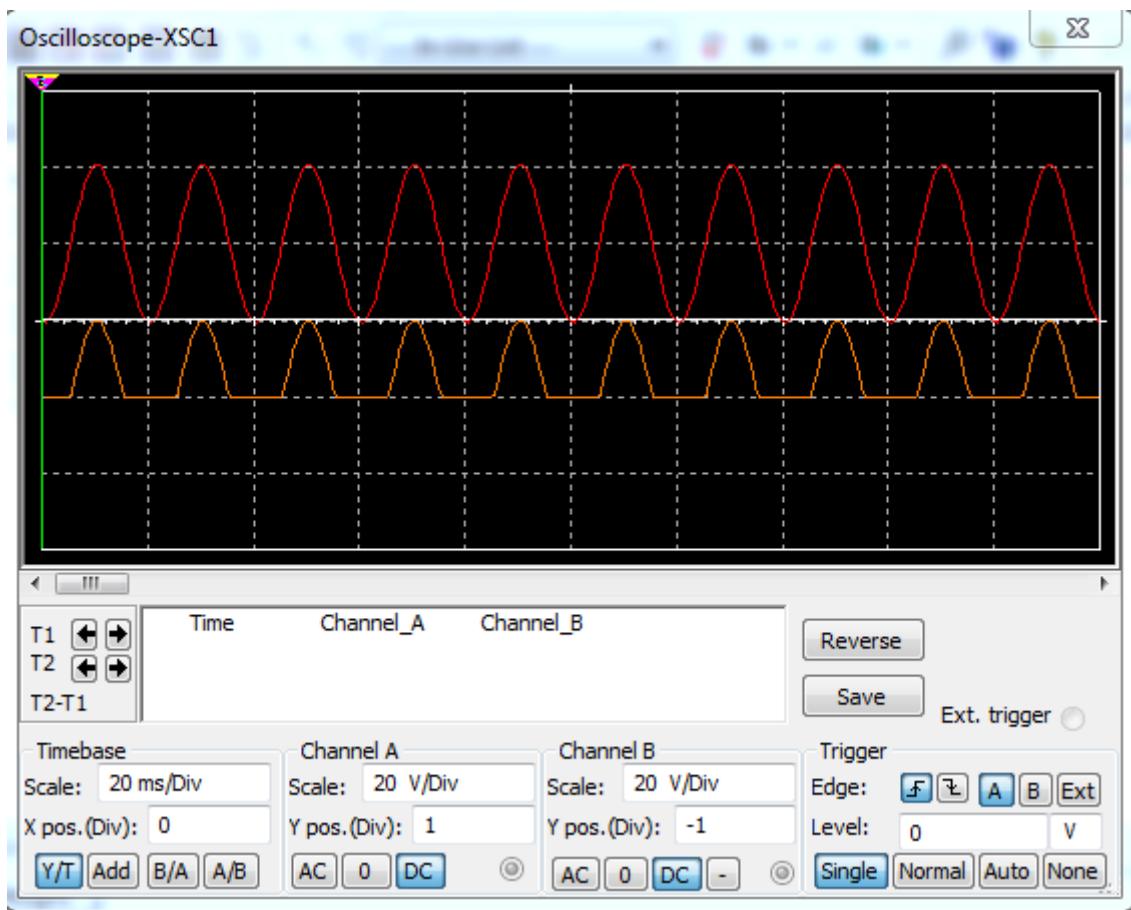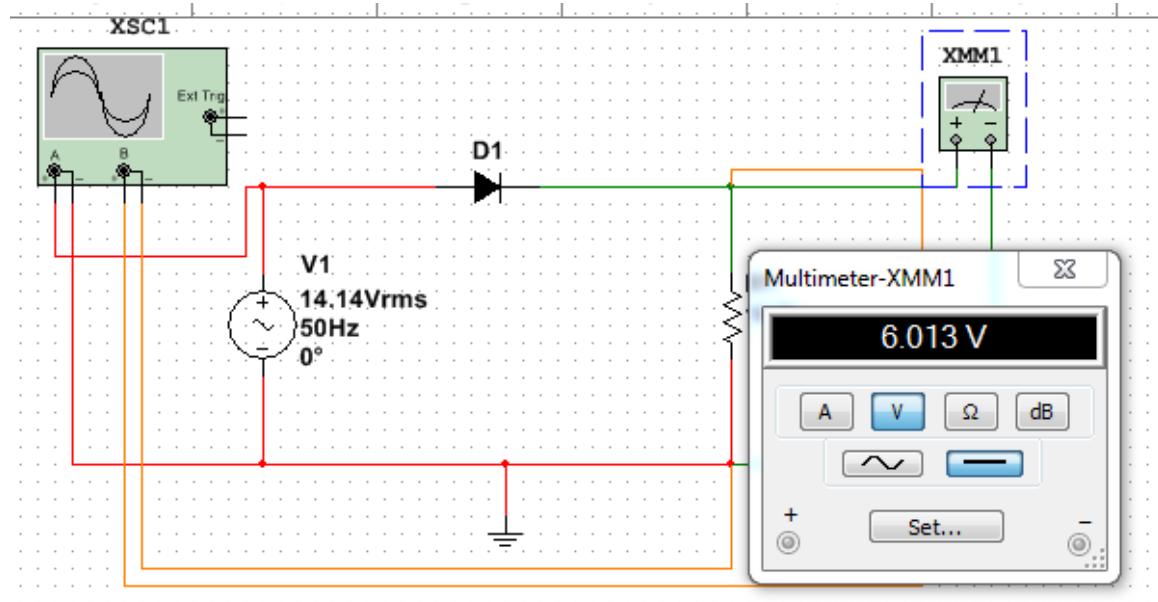

Discussions:

1. Why is there a difference between the peak of the input signal and the output signal?
2. What is the output Dc voltage?
3. What are the disadvantages of this circuit?
4. What is the basic purpose of this circuit in electrical devices?
5. How can we improve this circuit?

Part Two: Full-wave Rectifier

AIM: To study the input signal in the diode and the output signal from it, then calculate the output d.c voltage.

Apparatus: Full Wave Bridge (FWB) type 1B4B42, A.C power source = (14.14 rms and 50 Hz), Resistance = 1 kΩ, Ground, Oscilloscope and Multimeter.

Circuit diagram:

